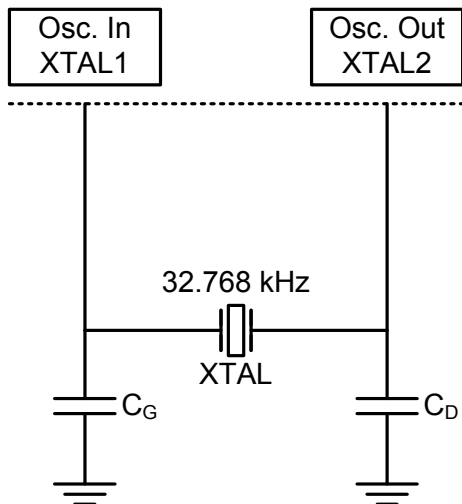


Pierce Oscillator

Design and Crystal
Recommendations

Atmel
ATmega169

ATmega169



Oscillator Design Check

Test Conditions			
Power Supply Voltage V_{DD}	1.8	2.7	V
Load Capacitors C_D / C_G	9 / 9		pF
Results			
Effective Load Capacitance	12.9	11.3	pF
Oscillation Allowance	>500	>500	k Ω
Oscillator Output Voltage AC	625	695	mV _{RMS}
Drive Level	0.435	0.385	μ W
Startup Time	250	200	ms
Overtone Mode Suppression	Safe		----

Recommendation

Crystal		
Crystal Type	MS3V-T1R / CC7V-T1A	
Frequency	32.768	kHz
Load Capacitance C_L	12.5	pF
Tolerance	+/-20	ppm
Oscillator Design		
C_D	9	pF
C_G	9	pF

Remarks

The ATmega169 consists of a self limiting Pierce Oscillator.

Placing $C_D = 9$ pF and $C_G = 9$ pF load capacitors on each side of the crystal results in an effective load capacitance of 12.9 pF at $V_{DD} = 1.8$ V and 11.3 pF at $V_{DD} = 2.7$ V (including board stray capacitances) which are good matches for a crystal specified for $C_L = 12.5$ pF.

The oscillator circuit provides an oscillation allowance greater than 500 k Ω ; this allows the safe use of smallest SMD quartz crystals ($ESR \leq 100$ k Ω).

Date: October 2010

Revision N°: 1.0


Page 1/5

In accordance with our policy of continuous development and improvement,
Micro Crystal reserves the right to modify specifications or design-recommendations without prior notice.
The recommendations stated above are based on measured-results, respecting the "oscillator design rules".
Micro Crystal makes no representation or warranty for information in this "Design and Crystal Recommendations".

Headquarters: Micro Crystal AG
Mühlestrasse 14
CH-2540 Grenchen
Switzerland


Tel. +41 32 655 82 82
Fax +41 32 655 82 83
Internet www.microcrystal.com
Email sales@microcrystal.com

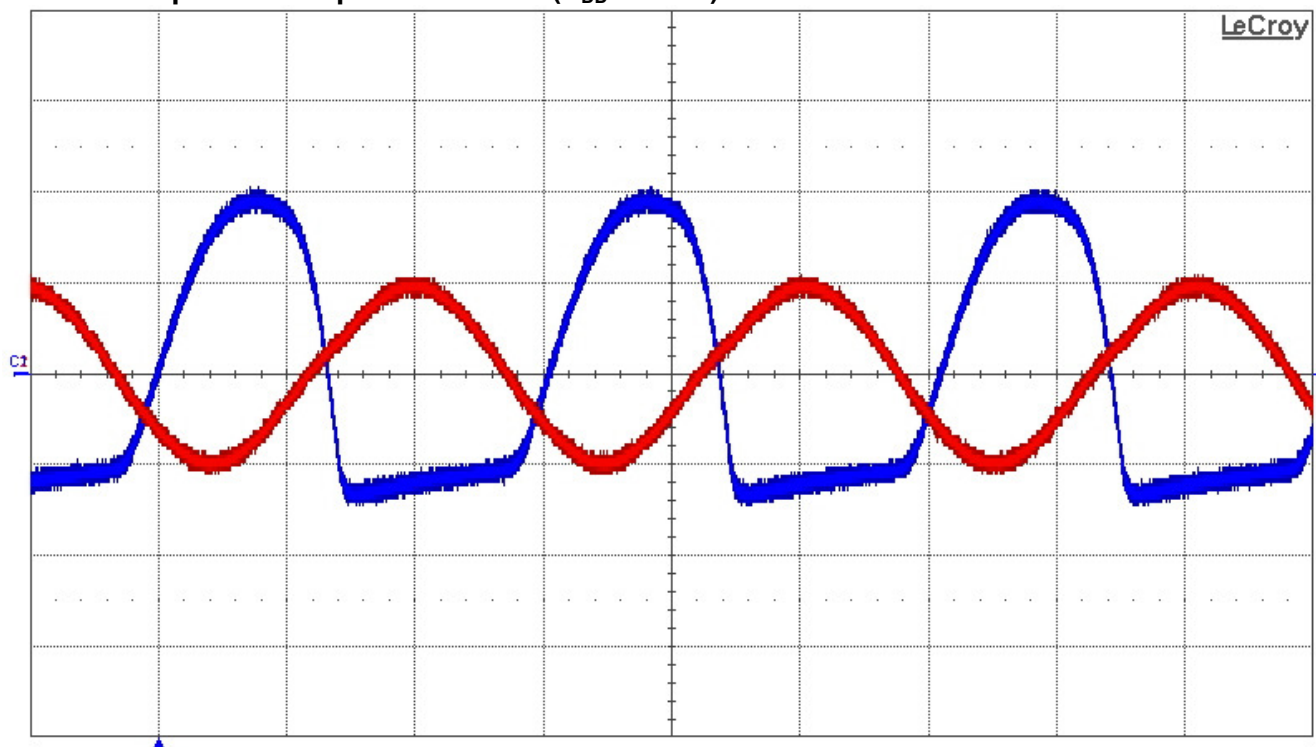Oscillator Input and Output waveforms ($V_{DD} = 1.8\text{ V}$):




■ C1: Osc. Out (500 mV/div - AC) ■ C2: Osc. In (500 mV/div - AC) Time base: 10 $\mu\text{s}/\text{div}$

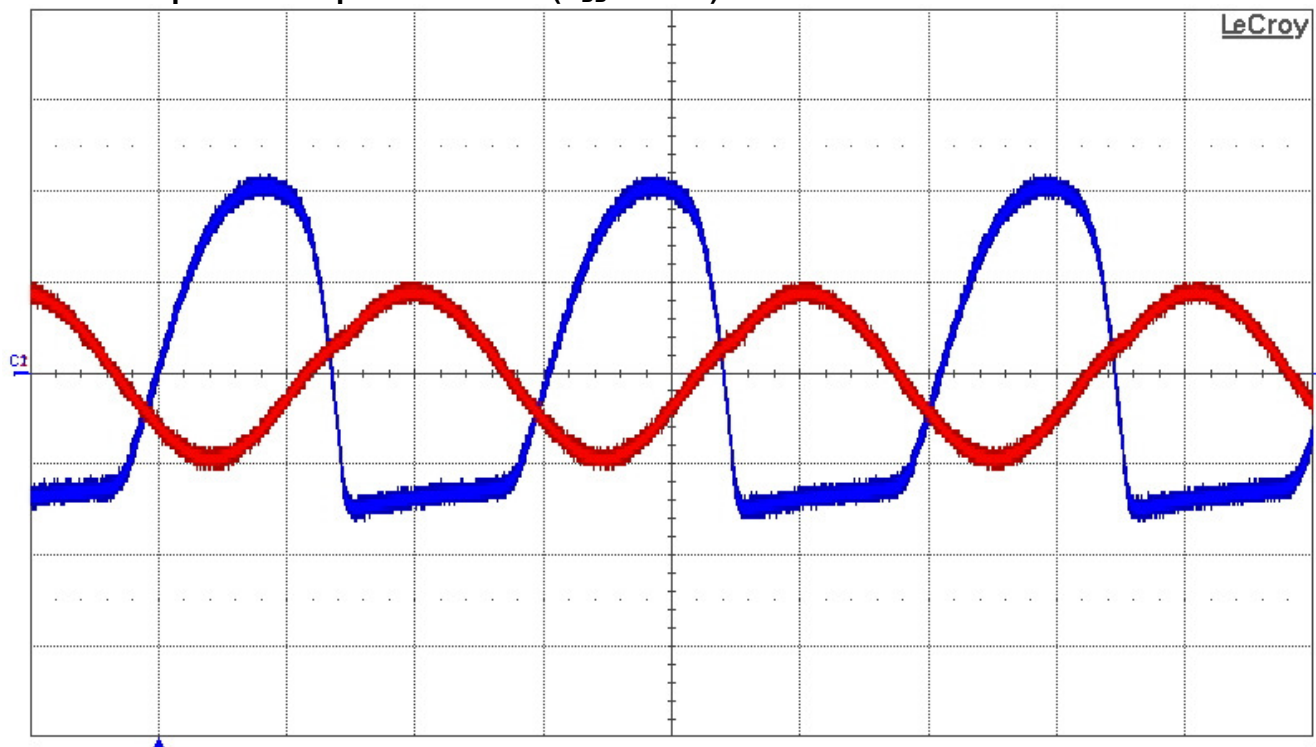Oscillator Input and Output waveforms ($V_{DD} = 2.7\text{ V}$):




■ C1: Osc. Out (500 mV/div - AC) ■ C2: Osc. In (500 mV/div - AC) Time base: 10 $\mu\text{s}/\text{div}$

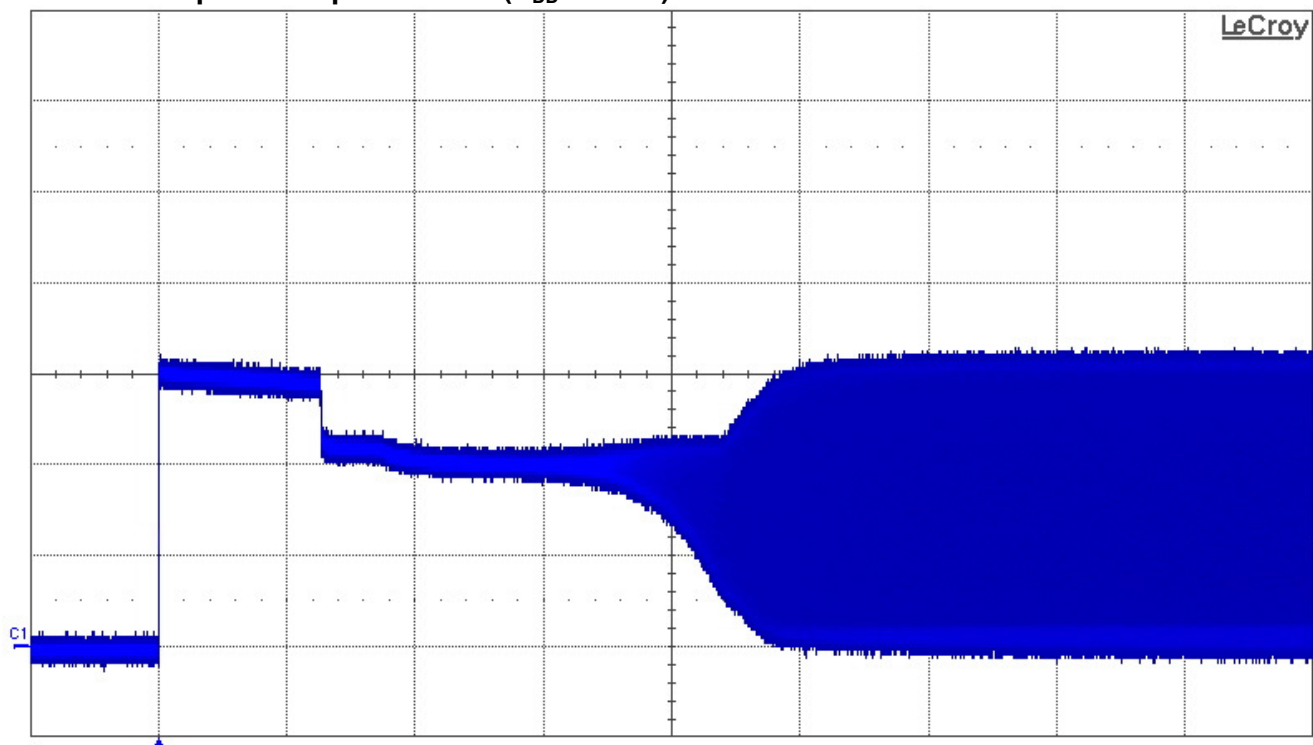Oscillator Output startup waveform ($V_{DD} = 1.8\text{ V}$):




■ C1: Osc. Out (500 mV/div - DC) Time base: 50 ms/div

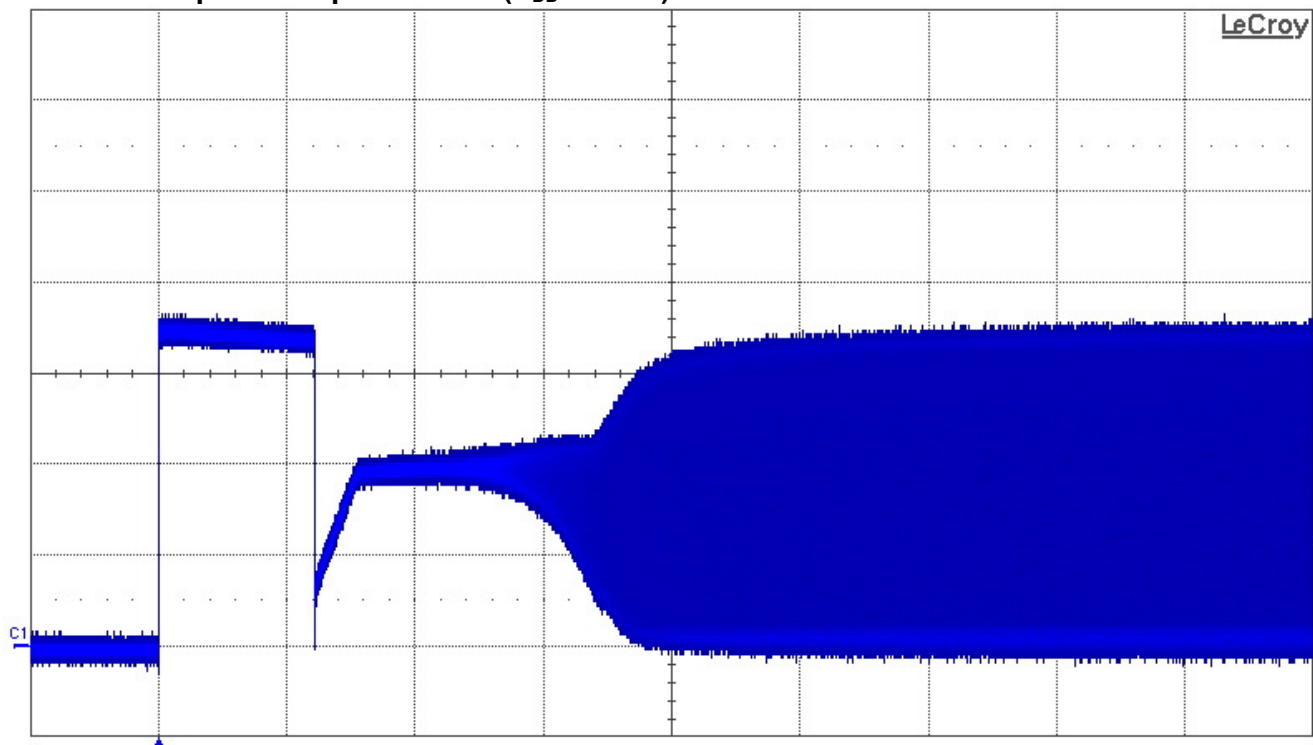Oscillator Output startup waveform ($V_{DD} = 2.7\text{ V}$):




■ C1: Osc. Out (500 mV/div - DC) Time base: 50 ms/div

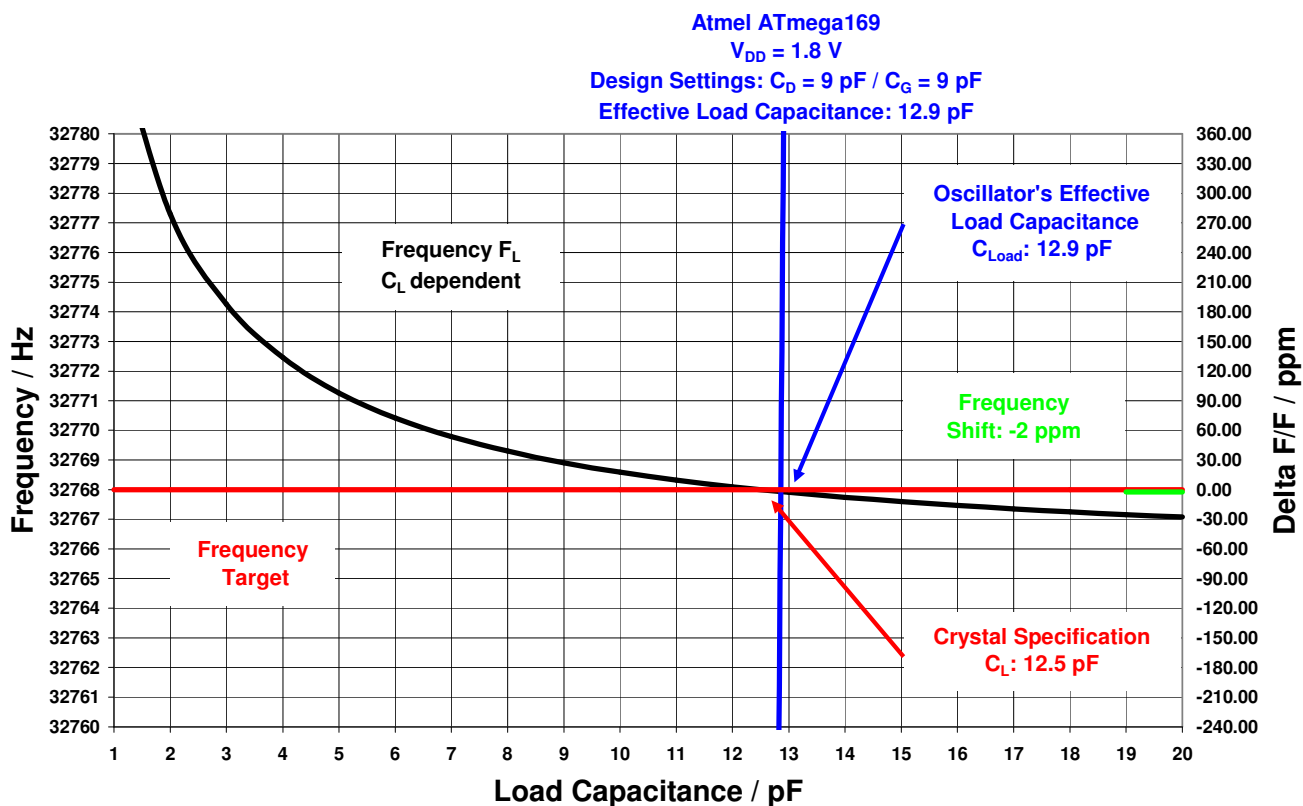Crystal matching chart ($V_{DD} = 1.8\text{ V}$):



As shown in the chart above, an effective load capacitance of 12.9 pF results in a frequency offset of -2 ppm using a MS3V-T1R crystal specified for $C_L = 12.5\text{ pF}$.

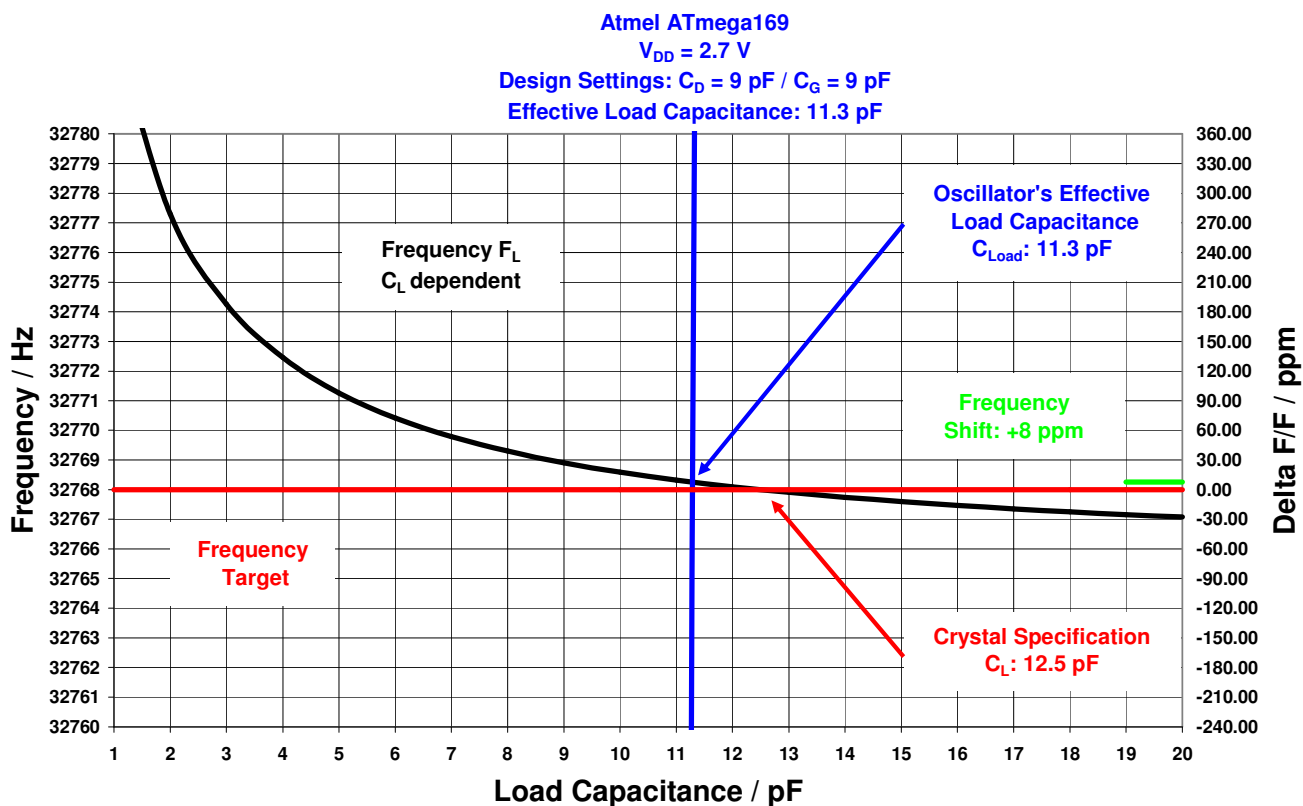Crystal matching chart ($V_{DD} = 2.7\text{ V}$):



As shown in the chart above, an effective load capacitance of 11.3 pF results in a frequency offset of +8 ppm using a MS3V-T1R crystal specified for $C_L = 12.5\text{ pF}$.