

Using the MCP16311/2 Synchronous Buck Converter Design Analyzer

Author: Mihai Tanase
Microchip Technology Inc.

INTRODUCTION

As increasingly more electronic equipment is developed in different fields of interest, and demands for longer run time and higher efficiency escalate, electrical system design engineers are now facing the difficulties of developing better and more efficient power supplies that can meet the requirements and standards in the industry.

Unfortunately, in many cases, the power supply design process is among the most troublesome parts of the project and requires a lot of time and effort.

In order to help engineers cope with the complexity of developing the power supplies best suitable for their design, IC manufacturers are providing power supply design tools, such as the Microchip Technology Incorporated MCP16311/2 Design Analyzer. This tool represents a superior alternative to the trial-and-error approach, which is both time and resource consuming as it involves repeatedly developing and testing prototypes until satisfactory results are obtained.

A design tool can help choose the best components and can provide an insight into how the power supply is going to behave under different conditions. By doing so, it provides valuable information long before receiving the actual board from the factory.

The Microchip MCP16311/2 Design Analyzer is a Microsoft® Excel®-based tool that calculates and recommends the most suitable components for user-specific applications. Furthermore, it has the option of tuning your external components in order to get the best results. By using the components and conditions specified in the input cells, the MCP16311/2 Design Analyzer can estimate the efficiency and frequency response of the power supply.

SYNCHRONOUS BUCK CONVERTER

Figure 1 shows an idealized version of a buck converter. In a traditional converter, the S_2 switch would have been a diode. This is still practiced in many of today's buck converters, as it offers increased simplicity in terms of control while being cost effective at the same time.

Although such an asynchronous solution may seem simpler and cheaper, it can also prove ineffective, especially when targeting low output voltages.

For this reason, a synchronous solution was developed which involves replacing the S_2 switch with a MOSFET, thus increasing efficiency and output current capabilities.

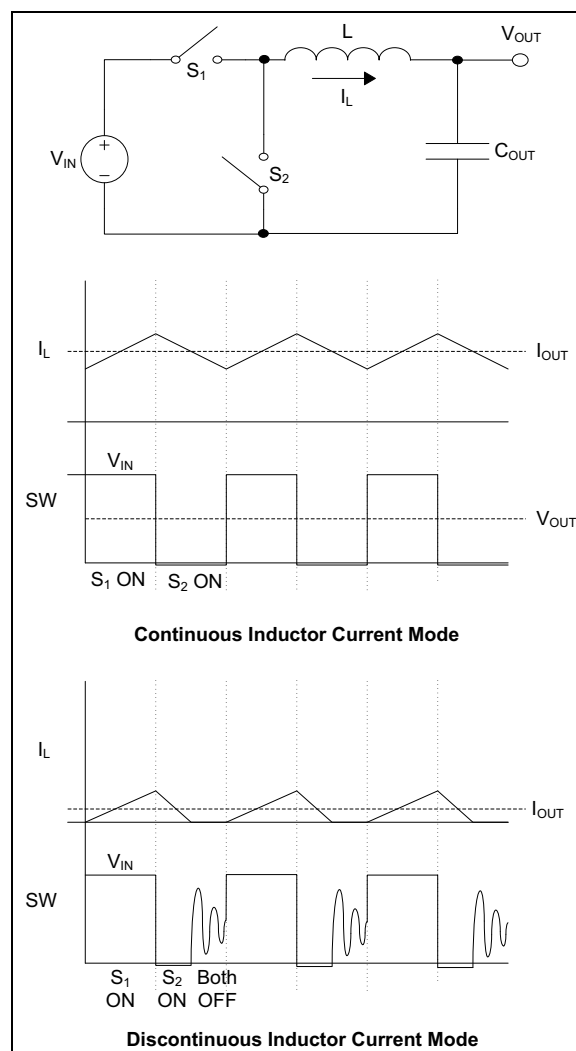


FIGURE 1: Buck Converter - Topology and Waveforms.

The basic operation of the buck converter can be illustrated by looking at the two current paths represented by the state of the two switches:

- S_1 - the high-side switch
- S_2 - the low-side switch

When the high-side switch is turned on, a DC voltage is applied to the inductor equal to $V_{IN} - V_{OUT}$, resulting in a positive linear ramp of inductor current.

Conversely, when the high-side switch turns off and the low-side switch turns on, the applied inductor voltage is equal to $-V_{OUT}$, which results in a negative linear ramp of inductor current.

In order to make sure there is no shoot-through current, a dead time where both switches are off is implemented between the high-side switch turning off and the low-side switch turning on and vice-versa.

A buck converter operates in Continuous Inductor Current mode if the current through the inductor never falls to zero during the commutation cycle. Provided that the inductor current reaches zero, the buck converter operates in Discontinuous Inductor Current mode.

The two modes of operation are represented in [Figure 1](#).

Typically, by using a synchronous solution, the converter is forced to run in Continuous Inductor Current mode no matter the load at the output. This, in turn, causes losses at low loads as the output is being discharged.

One solution to this problem, which is also applied in the design of the MCP16311/2, is to use a zero-current comparator. This comparator monitors the current through the low-side switch, and when it reaches zero, the switch is turned off.

This feature is called *diode emulation* and, by implementing it, the converter will have the advantages of both Synchronous and Asynchronous modes of operation.

MCP16311/2 SHORT OVERVIEW

The MCP16311/2 device is a compact, high-efficiency, fixed frequency, synchronous step-down DC-DC converter in an 8-pin MSOP or 2x3 TDFN package that operates using input voltage sources of up to 30V.

Integrated features include a high-side as well as a low-side switch, fixed frequency peak current mode control, internal compensation, overcurrent limit and undervoltage lockout overtemperature protection.

High converter efficiency is achieved by integrating the low-resistance, high-speed low-side and high-side switches as well as associated drive circuitry.

In order to deliver high efficiency over the entire load range, starting from $\sim 100 \mu\text{A}$ up to 1A, the MCP16311 can run in both Pulse-Width Modulation (PWM) and Pulse-Frequency Modulation (PFM) mode. It switches to PFM mode for light load conditions and for large buck conversion ratios. The MCP16312 can run in PWM-only mode.

MCP16311/2 Features

- Input Voltage Range: 4.4V to 30V with UVLO at 4.1V to start and 3.6V to stop
- Up to 1A Output Current Capability
- Integrated low-side ($R_{DS(ON)}$: 170 m Ω) and Integrated high-side ($R_{DS(ON)}$: 300 m Ω)
- Switching Frequency: 500 kHz
- Reference Voltage: 0.8V
- Adjustable Output Voltage from 2V to 24V
- Automatic Pulse-Frequency Modulation/Pulse-Width Modulation (PFM/PWM) for the MCP16311 or PWM-only operation for the MCP16312
- Low Device Quiescent Current: 44 μA (non switching) for MCP16311
- Low Device Shutdown Current: 4 μA
- Soft-start: 300 μs
- Peak Current Mode Control
- Thermal Shutdown: 150°C with 25°C hysteresis

PFM/PWM Operation

In order to further increase the efficiency at light loads, in addition to diode emulation, the MCP16311 features a Pulse-Frequency Modulation (PFM) mode of operation.

When in this mode, compared to the traditional Pulse-Width Modulation (PWM), the MCP16311 increases the output voltage just up to the point after which it enters a “sleep” mode. During this dormant state, the device stops switching and consumes only 44 μA of the input. When the output voltage drops below its nominal value, the device restarts switching and brings the output back into regulation.

An instance of PFM operation is represented in [Figure 2](#) and can be easily identified by the triangular waveform at the output of the converter.

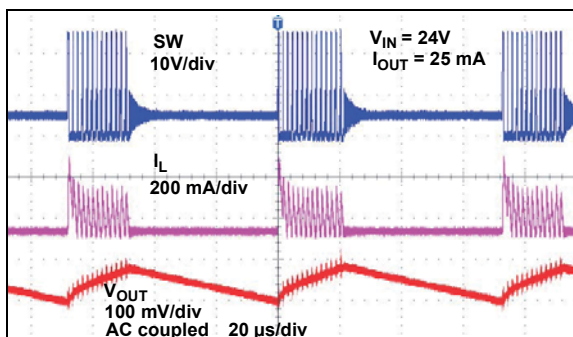


FIGURE 2: MCP16311 - PFM Operation.

The PFM mode of operation considerably increases the efficiency of the converter at light loads, while also adding a lower-frequency component at the output which varies with the input voltage, output voltage and output current.

Once the output load increases, the converter transitions to normal PWM operation. The threshold point is determined by the input-to-output voltage ratio and by the output current.

Because of the triangular waveform at the output, in more sensitive applications, the use of the MCP16312 is recommended because it runs in PWM mode.

MCP16311/2 DESIGN ANALYZER

The MCP16311/2 Design Analyzer is a simple Excel tool that provides the user with a classic interface, laid out as predefined cells, in which various system parameters have to be defined.

In order to separate and define the fields clearly, the cells have been color coded.

Figure 3 provides an overview of the MCP16311/2 Design Analyzer.

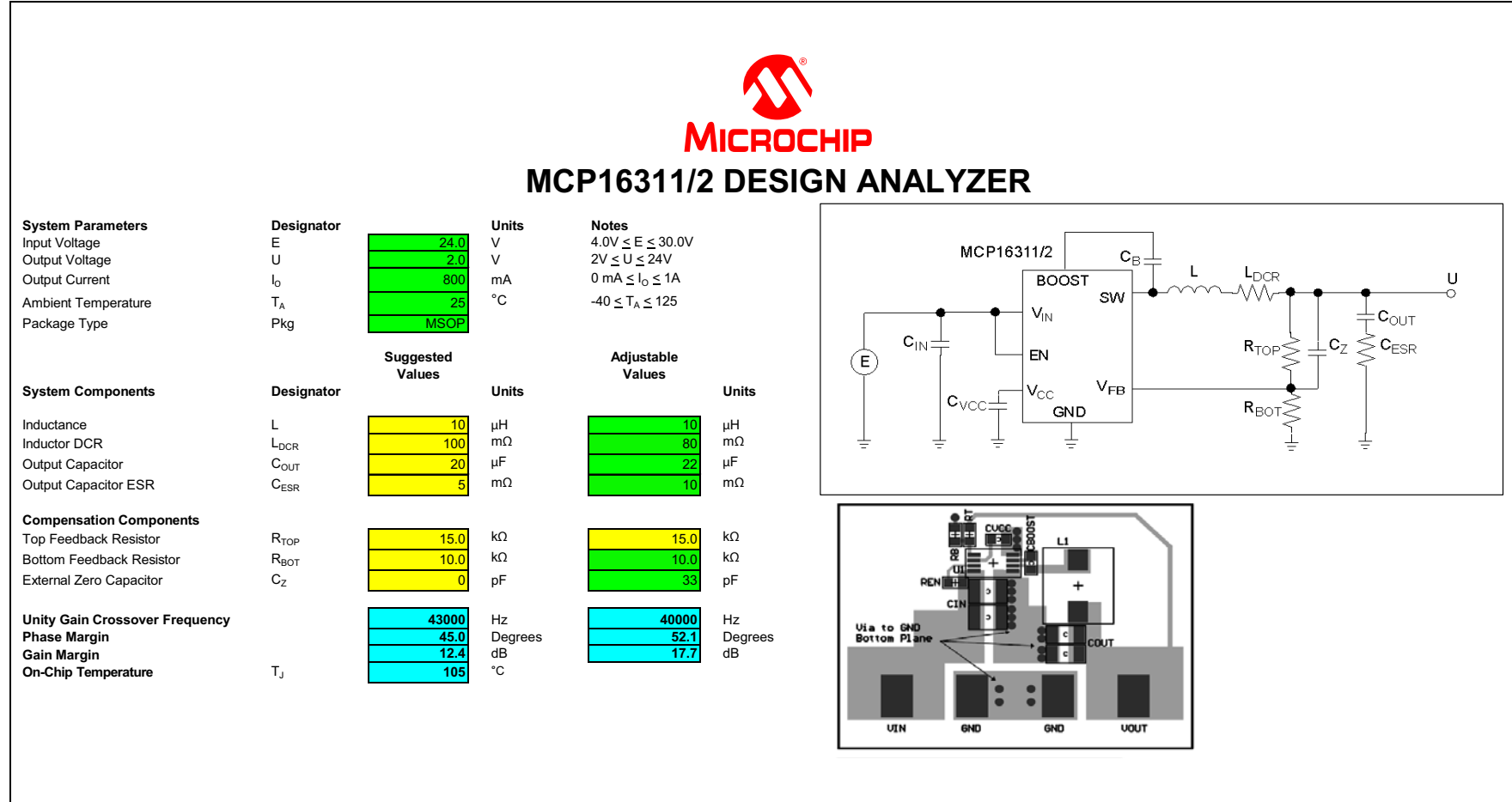


FIGURE 3: MCP16311/2 Design Analyzer - Overview.

System Parameters

The cells corresponding to system input parameters are marked in *green* as shown in [Table 1](#). In this field, the user has to define the input voltage, the output voltage, the maximum output current, the ambient temperature and the desired package type. Note that the system parameters are limited to the minimum and maximum values recommended for this section.

System Components

Based on the parameters input by the user in the [System Parameters](#) field, the Design Analyzer calculates the recommended inductor, output capacitor and feedback resistor values. These are displayed in *yellow* as shown in [Table 2](#).

Recommended Layout

Depending on the package type and ambient temperature selected by the user, the Design Analyzer will estimate the temperature of the switchers. On the right of the Design Analyzer, a typical schematic along with a recommended layout for each package type will be displayed.

Efficiency Estimation

In order for the results provided by the Design Analyzer to be as realistic as possible, the user has the choice of trying alternative component values based on the suggested values, and assessing their overall effect on the system. All efficiency and stability analysis is done depending on the user-input adjustable values to minimize errors and ensure the best possible representation of the system's performance.

For the MCP16312, the PWM-only version, the Design Analyzer estimates the efficiency over the entire load range depending on the system parameters and user-selected system components. Because the PFM behavior is affected by both input voltage and output voltage as well as output current, it is difficult to estimate efficiency when running in PFM mode.

For efficiency at low loads in the PFM region, please refer to the MCP16311/2 Data Sheet – “30V Input, 1A Output, High-Efficiency, Integrated Synchronous Switch Step-Down Regulator” (DS20005255).

At this point, the designer can tune the system components in order to achieve the targeted efficiency. This process is represented in [Figure 4](#).

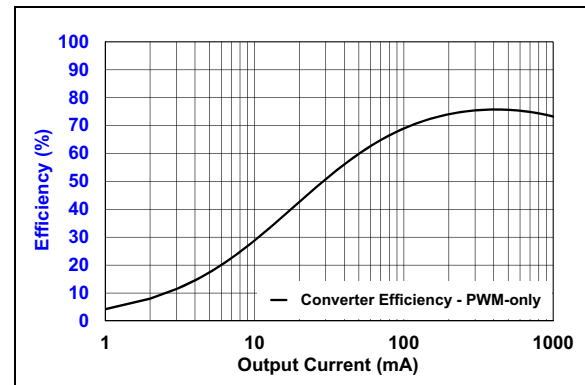


FIGURE 4: MCP16312 - Converter Efficiency

Note: The efficiency estimation included in the design tool should not replace the actual measurement of the efficiency, as this might vary according to input voltages, loads, and different external conditions such as temperature.

Peak Current Mode Control Architecture

The MCP16311/2 integrates a Peak Current Mode Control Architecture, which is used to provide better response to load and line transients. Compared to the Voltage Mode Control, which uses an internal sawtooth generator, the Peak Current Mode Control uses the inductor current, which is compared to the error voltage, to form the duty cycle.

Through this control approach, the order of the system is reduced from a 2nd order to a 1st order, making the compensation much easier and the dynamic performance much better than a traditional voltage mode control.

AN1960

Converter Bode Plot

The design tool provides information about the expected stability and dynamic performance of the converter through the bode plot of the closed loop system.

A bode plot is a graph of a transfer function, and it represents the magnitude (expressed in decibels) and phase (expressed in degrees) of the transfer function plotted on a logarithmic frequency scale, as shown in Figure 5.

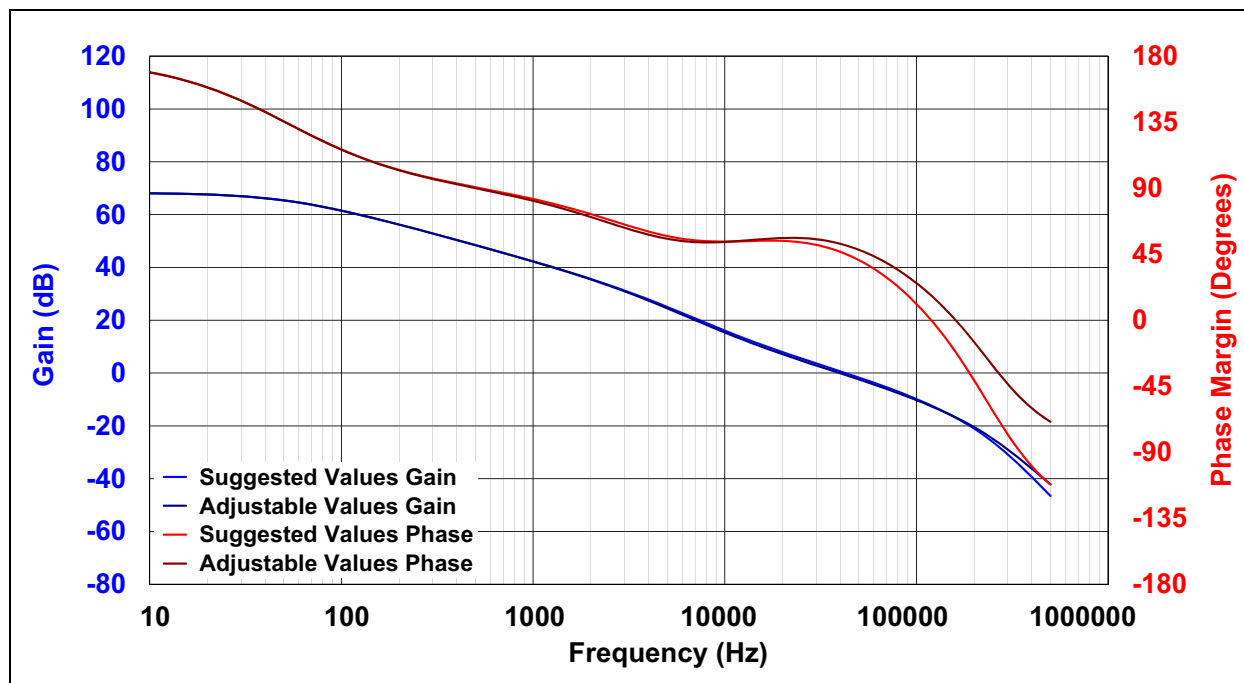


FIGURE 5: MCP16311/2 - Converter Bode Plot.

In order to estimate the stability and dynamic performance through the bode plots, three parameters have to be considered:

- **Crossover Frequency:** the system crossover frequency is the point where the gain of the system becomes 0 dB. A higher crossover frequency equals better dynamic performance and better transient response. However, due to possible noise issues, the crossover frequency cannot be set infinitely high.
- **Phase Margin:** in a closed-loop system that uses negative feedback, the system phase margin is defined by the difference between the phase at the crossover frequency and 0 degrees. This parameter is directly related to the stability of the closed-loop system.
- **Gain Margin:** the system gain margin is defined as the amount of gain that has to be added to the system gain to reach 0 dB, calculated at the point where the phase reaches 0 degrees. This parameter is also directly related to stability, and it indicates how far the system is from becoming unstable.

For the system to be considered stable in real-life situations where noise and high-order effects may occur, the following two conditions have to be concurrently satisfied:

- phase margin ≥ 45 degrees
- gain margin ≥ 6 dB.

The higher the value, the more stable the system is. However, by over-increasing these two parameters, the crossover frequency decreases, making the system slower and with poor dynamic response to external perturbations.

By modifying the external components (the inductor, capacitor or feedback loop), the user can tune the frequency response of the system.

STEP-BY-STEP DESIGN APPLICATION

This section presents a design example using the MCP16311/2 Design Analyzer. The required project has the following input parameters:

TABLE 1: MCP16311/2 - INPUT PARAMETERS

System Parameters	Designator	Suggested Values	Units	Notes
Input Voltage	E	24	V	$4.0V \leq E \leq 30.0V$
Output Voltage	U	2	V	$2V \leq U \leq 24V$
Output Current	I _O	800	mA	$0 \text{ mA} \leq I_O \leq 1A$
Ambient Temperature	T _A	25	°C	$-40 \leq T_A \leq 125$
Package Type	Pkg	MSOP		

Based on these input parameters, the Design Analyzer calculates the recommended values of the external components for both the power train and the feedback loop. At this point, the user has the possibility to fine-tune the component values in order to get more precise results.

In this particular example, the inductor DCR and the capacitor parameter have been modified. In order to gain more phase margin, the external zero capacitor has been added, as well.

TABLE 2: MP16311/2 - SYSTEM AND COMPENSATION COMPONENTS

	Designator	Suggested Values	Adjustable Values	Units
System Components				
Inductance	L	10	10	μH
Inductor DCR	L _{DCR}	100	80	mΩ
Output Capacitor	C _{OUT}	20	22	μF
Output Capacitor ESR	C _{ESR}	5	10	mΩ
Compensation Components				
Top Feedback Resistor	R _{TOP}	15.0	15.0	kΩ
Bottom Feedback Resistor	R _{BOT}	10.0	10.0	kΩ
External Zero Capacitor	C _Z	0	33	pF

TABLE 3: MCP16311/2 - STABILITY ANALYSIS SUMMARY

Crossover Frequency	48000	40000	Hz
Phase Margin	42.2	52.1	Degrees
Gain Margin	16.9	17.7	dB
On-Chip Temperature	105		°C

Note: In the blue cells, the stability analysis summary (for both the suggested value and the adjustable value) is displayed.

CONCLUSION

The MCP16311/2 design analyzer provides the user with a tool to estimate the static and dynamic behavior of the MCP16311/2 synchronous buck converter.

By using this design tool, the engineering cost and schedule time can be reduced as the optimized final solution is reached in fewer iterations.

However, the design analyzer should not substitute proper in-system verification and validation, but rather help facilitate these processes.

AN1960

NOTES:

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable.”

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, FlashFlex, flexPWR, JukeBlox, KEELOQ, KEELOQ logo, Klear, LANCheck, MediaLB, MOST, MOST logo, MPLAB, OptoLyzer, PIC, PICSTART, PIC³² logo, RightTouch, SpyNIC, SST, SST Logo, SuperFlash and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

The Embedded Control Solutions Company and mTouch are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, BodyCom, chipKIT, chipKIT logo, CodeGuard, dsPICDEM, dsPICDEM.net, ECAN, In-Circuit Serial Programming, ICSP, Inter-Chip Connectivity, KlearNet, KlearNet logo, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, RightTouch logo, REAL ICE, SQI, Serial Quad I/O, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

Silicon Storage Technology is a registered trademark of Microchip Technology Inc. in other countries.

GestIC is a registered trademarks of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2015, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-63277-558-0

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949 ==

Microchip received ISO/TS-16949:2009 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



MICROCHIP

Worldwide Sales and Service

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199

Tel: 480-792-7200

Fax: 480-792-7277

Technical Support:

[http://www.microchip.com/
support](http://www.microchip.com/support)

Web Address:

www.microchip.com

Atlanta

Duluth, GA

Tel: 678-957-9614

Fax: 678-957-1455

Austin, TX

Tel: 512-257-3370

Boston

Westborough, MA

Tel: 774-760-0087

Fax: 774-760-0088

Chicago

Itasca, IL

Tel: 630-285-0071

Fax: 630-285-0075

Cleveland

Independence, OH

Tel: 216-447-0464

Fax: 216-447-0643

Dallas

Addison, TX

Tel: 972-818-7423

Fax: 972-818-2924

Detroit

Novi, MI

Tel: 248-848-4000

Houston, TX

Tel: 281-894-5983

Indianapolis

Noblesville, IN

Tel: 317-773-8323

Fax: 317-773-5453

Los Angeles

Mission Viejo, CA

Tel: 949-462-9523

Fax: 949-462-9608

New York, NY

Tel: 631-435-6000

San Jose, CA

Tel: 408-735-9110

Canada - Toronto

Tel: 905-673-0699

Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office

Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon

Hong Kong

Tel: 852-2943-5100

Fax: 852-2401-3431

Australia - Sydney

Tel: 61-2-9868-6733

Fax: 61-2-9868-6755

China - Beijing

Tel: 86-10-8569-7000

Fax: 86-10-8528-2104

China - Chengdu

Tel: 86-28-8665-5511

Fax: 86-28-8665-7889

China - Chongqing

Tel: 86-23-8980-9588

Fax: 86-23-8980-9500

China - Dongguan

Tel: 86-769-8702-9880

China - Hangzhou

Tel: 86-571-8792-8115

Fax: 86-571-8792-8116

China - Hong Kong SAR

Tel: 852-2943-5100

Fax: 852-2401-3431

China - Nanjing

Tel: 86-25-8473-2460

Fax: 86-25-8473-2470

China - Qingdao

Tel: 86-532-8502-7355

Fax: 86-532-8502-7205

China - Shanghai

Tel: 86-21-5407-5533

Fax: 86-21-5407-5066

China - Shenyang

Tel: 86-24-2334-2829

Fax: 86-24-2334-2393

China - Shenzhen

Tel: 86-755-8864-2200

Fax: 86-755-8203-1760

China - Wuhan

Tel: 86-27-5980-5300

Fax: 86-27-5980-5118

China - Xian

Tel: 86-29-8833-7252

Fax: 86-29-8833-7256

ASIA/PACIFIC

China - Xiamen

Tel: 86-592-2388138

Fax: 86-592-2388130

China - Zhuhai

Tel: 86-756-3210040

Fax: 86-756-3210049

India - Bangalore

Tel: 91-80-3090-4444

Fax: 91-80-3090-4123

India - New Delhi

Tel: 91-11-4160-8631

Fax: 91-11-4160-8632

India - Pune

Tel: 91-20-3019-1500

Japan - Osaka

Tel: 81-6-6152-7160

Fax: 81-6-6152-9310

Japan - Tokyo

Tel: 81-3-6880-3770

Fax: 81-3-6880-3771

Korea - Daegu

Tel: 82-53-744-4301

Fax: 82-53-744-4302

Korea - Seoul

Tel: 82-2-554-7200

Fax: 82-2-558-5932 or

82-2-558-5934

Malaysia - Kuala Lumpur

Tel: 60-3-6201-9857

Fax: 60-3-6201-9859

Malaysia - Penang

Tel: 60-4-227-8870

Fax: 60-4-227-4068

Philippines - Manila

Tel: 63-2-634-9065

Fax: 63-2-634-9069

Singapore

Tel: 65-6334-8870

Fax: 65-6334-8850

Taiwan - Hsin Chu

Tel: 886-3-5778-366

Fax: 886-3-5770-955

Taiwan - Kaohsiung

Tel: 886-7-213-7828

Taiwan - Taipei

Tel: 886-2-2508-8600

Fax: 886-2-2508-0102

Thailand - Bangkok

Tel: 66-2-694-1351

Fax: 66-2-694-1350

EUROPE

Austria - Wels

Tel: 43-7242-2244-39

Fax: 43-7242-2244-393

Denmark - Copenhagen

Tel: 45-4450-2828

Fax: 45-4485-2829

France - Paris

Tel: 33-1-69-53-63-20

Fax: 33-1-69-30-90-79

Germany - Dusseldorf

Tel: 49-2129-3766400

Germany - Munich

Tel: 49-89-627-144-0

Fax: 49-89-627-144-44

Germany - Pforzheim

Tel: 49-7231-424750

Italy - Milan

Tel: 39-0331-742611

Fax: 39-0331-466781

Italy - Venice

Tel: 39-049-7625286

Netherlands - Drunen

Tel: 31-416-690399

Fax: 31-416-690340

Poland - Warsaw

Tel: 48-22-3325737

Spain - Madrid

Tel: 34-91-708-08-90

Fax: 34-91-708-08-91

Sweden - Stockholm

Tel: 46-8-5090-4654

UK - Wokingham

Tel: 44-118-921-5800

Fax: 44-118-921-5820

01/27/15