

Introduction

A quartz crystal is a very stable and accurate resonator. Quartz crystals have been used for almost a century to provide a frequency reference in electronic circuits. In the 1940s, the manufacturing of quartz crystals was industrialized due to a sudden need for reliable wireless communication during WWII. Prior to that, crystals were mostly used by radio amateurs and it was with their assistance that the quartz crystal industry in the US was built-up during this timeframe. At that time, natural quartz was used and only a few mines provided the required purity for a good-performing quartz crystal. Today, synthetic quartz – with its higher purity levels – has replaced natural quartz as a key component in timing and communication applications. This application note will explain how to choose or specify a quartz crystal for use with a Micrel timing IC ([Figure 1](#)).

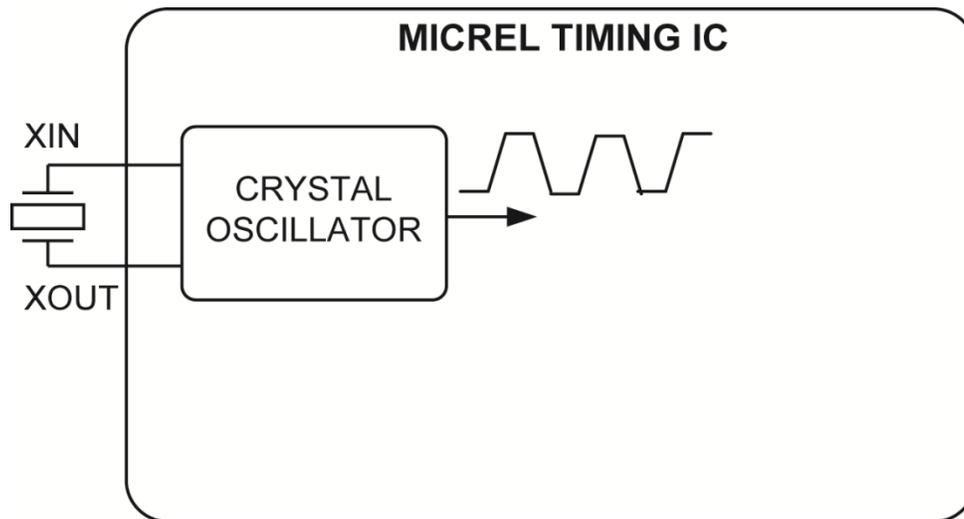


Figure 1. Example of Using a Crystal in a Micrel IC

How the Crystal Works

The crystal itself is passive and needs an electronic circuit – a crystal oscillator – to create a reference clock signal. To get the crystal to vibrate, electrodes are placed on the quartz surface. Quartz has piezo electric properties and a voltage between two electrodes makes the crystal change its shape. An alternative approach also works: applying pressure to the crystal to change its shape will result in an electrical voltage appearing between two electrodes. This interaction between electrical voltage and mechanical shape causes useful electrical impedance behavior at the mechanical resonance of the piece of quartz. The crystal absorbs electrical energy from an AC voltage at the mechanical resonance. In other words, the electrical impedance drops at the mechanical resonance so a crystal can be used as a filter to pass the resonance frequency through. An oscillator circuit uses this to build a reference clock signal at this resonance frequency.

An example of the traditional construction of a quartz crystal is illustrated in [Figure 2](#). In this example, the quartz crystal has the shape of a round disk. An electrode is placed on both sides of the disk to apply an electrical voltage. To preserve the frequency accuracy we need to avoid the quartz crystal becoming dirty or the electrode oxidizing. The crystal is typically placed in a hermetic enclosure to keep it clean. [Figure 2](#) shows a metal can enclosure where the lid is removed. Surface-mountable ceramic enclosures with smaller dimensions have become much more common.

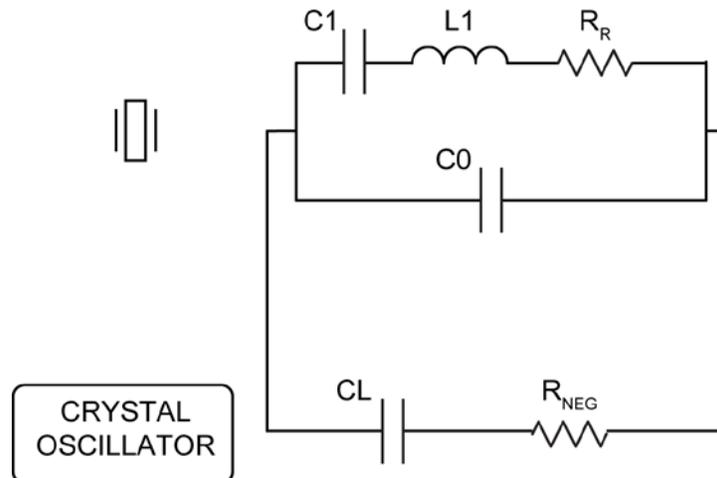


Figure 2. Traditional Construction of a Quartz Crystal

Most crystals, including the crystal displayed in [Figure 2](#), vibrate the thickness of a disk. Note that the thinner the disk is, the higher the frequency it will vibrate at. To manufacture a crystal with a specific frequency, the thickness must be carefully adjusted to achieve the target frequency. The final calibration is done by etching a small amount of metal (typically silver) away from the electrode to reduce its mass and force the frequency rise. The crystal frequency is monitored during the etching – or ion beam tuning – and is stopped when it has reached its target.

Micrel Crystals

Many Micrel timing ICs use a quartz crystal for the frequency reference. There are certain parameters of a quartz crystal that need to match the parameters of the oscillator circuit for the best frequency accuracy and most reliable operation. The parameters can be best pointed out in the electrical model for the quartz crystal and simplified model for the crystal oscillator, illustrated in [Figure 3](#).



Parameters:

C1 – Crystal motional capacitance.

L1 – Crystal motional inductance.

RR – Crystal resonance resistance.

CL – Oscillator load capacitance.

RNEG – Oscillator gain, presented as a resistance with a negative value.

Figure 3. Electrical Model for Quartz Crystal/Simplified Model for Crystal Oscillator

Table 1. Crystal Parameter Typical Values

| Parameter | Value | Notes |
|-----------------------------------|-----------------|--|
| C1 (Motional Capacitance) | 15fF ~ 25fF | Large metal can crystal. |
| | 1fF ~ 5fF | Small ceramic surface mount crystal or mesa crystal. |
| | 0.1fF ~ 2fF | Overtone crystals. |
| C0 (Parallel Capacitance) | 3pF ~ 5pF | Large metal can crystal. |
| | 0.5pF ~ 2pF | Small ceramic surface mount crystal or mesa crystal. |
| ESR (Effective Series Resistance) | 5Ω ~ 15Ω | Large metal can crystal. |
| | 15Ω ~ 50Ω | Small ceramic surface mount crystal. |
| PD (Drive Level) | 500μW (maximum) | Large metal can crystal. |
| | 50μW (maximum) | Small ceramic surface mount crystal. |
| CL (Load Capacitance) | 12pF ~ 20pF | Low frequencies, 10MHz ~ 25MHz. |
| | 5pF ~ 12pF | Medium frequencies, 25MHz ~ 50MHz. |
| | 3pF ~ 5pF | High frequencies up to 200MHz with mesa crystals. |

Explanation of Parameters

C1 and L1

The motional capacitor (C1) represents the elasticity of quartz while the motional inductor (L1) represents the moving mass. As a result, the C1 and L1 circuit is the electrical resonating tank representation of the mechanical resonance in the quartz crystal. The value of C1 is important when trying to tune the frequency of the crystal through changing the load capacitance in the crystal oscillator. The larger the value of C1, the more frequency deviation from the same load capacitance variation will occur. For example, in a voltage-controlled XTAL oscillator (VCXO) as in Micrel's PL500, PL502, PL520, or PL586 series of products, this is important because the VCXO needs to have a specific frequency tuning range. If no frequency tuning is present, the value of C1 is less important. For variations in the load capacitance to have less of an effect on the frequency, a smaller value for C1 may be desirable. The value of L1 is not often specified. Instead, the frequency is specified and we can calculate L1 from C1 and the frequency.

Micrel may specify C1 in the event it is important to achieve a certain frequency tuning range. Where it is not specified, it is left to the crystal manufacturer to choose the best value based upon manufacturability.

R_R, ESR, and R_{NEG}

The resonance resistor (R_R) represents the losses in the crystal when it is resonating. The crystal oscillator's negative resistance will settle at a value that exactly cancels the positive crystal resonance resistance, causing a perpetual oscillation. The values of R_{NEG} and R_R in this circuit are not identical because of C0. In typical crystal specifications, a value identified as equivalent series resistance (ESR) is noted. This value is the exact opposite (positive) of the R_{NEG} value in the circuit and can be calculated from the R_R, C0, and CL values.

When the crystal oscillator is first turned on, the value of R_{NEG} needs to be much larger than the ESR to grow the oscillation signal quickly. A good rule of thumb is to have the R_{NEG} value equal to at least three times (3X) than ESR value to ensure reliable start-up of the crystal oscillator. When the oscillation amplitude has reached specific amplitude, the nonlinear properties of the oscillator amplifier will prevent the signal from growing further and the R_{NEG} value is effectively reducing to equal ESR value for perpetual oscillation. There are a variety of different methods for setting the oscillation amplitude where the crystal oscillator settles. Micrel can provide the value of R_{NEG} in its timing ICs and will specify the ESR or R_R to ensure a proper oscillator startup.

C0

C0 is the parallel – or holder – capacitance of the crystal. It is typically generated by the electrodes in the crystal. At frequencies not near a mechanical resonance of the crystal, the quartz crystal behaves like an ordinary capacitor with a few pico-Farads (pF) of capacitance. The C0 does not have a purpose; it is a parasitic capacitance in the crystal that only has a negative influence on the performance. Micrel can specify a maximum value so that C0 does not interfere too much with crystal oscillator startup or frequency tuning.

CL

The load capacitance (CL) is a property of the crystal oscillator. Its value influences the exact oscillation frequency of the oscillator with the crystal. To ensure frequency accuracy, crystals are calibrated to resonate at their nominal frequency with a specific load capacitance value. Micrel can specify the CL value of the crystal oscillator circuit in its timing IC to ensure the proper crystal can be selected. Theoretically, a crystal manufacturer can make any CL value although the most popular values are readily available with most distributors. It is possible to adjust a CL value with an additional capacitor in order to use a popular CL value crystal. Contact Micrel for advice on exactly how much adjustment a certain timing IC can tolerate.

With programmable clock generators like Micrel's PL610, PL611, and PL611s series, CL is programmable and can be customized to a specific crystal in combination with PCB trace capacitance.

FL

FL represents the load frequency where the crystal oscillator will oscillate. In relation to the crystal, it is the oscillation frequency specified at a certain value for the CL. The nominal frequency specified for a crystal will be this load frequency.

FS

The series resonance frequency (FS) of the crystal is determined by C1 and L1. FL is the frequency where the impedance of the crystal is the lowest and, therefore, easy to find with a network analyzer. Some oscillators can oscillate at this frequency, although it is not typical.

Parameter Interactions and Dependencies

The “perfect” crystal has a low R_R or ESR, a low C0 value, and a large C1 value in the event there is a need to tune the frequency. Unfortunately, this “perfect” crystal does not exist due to dependencies between the parameters. Increasing the size of the electrode effectively increases the value of C1 and decreases the value of R_R or ESR while also increasing the value of C0. Obviously, the size of the electrode is also limited by the total size of the quartz disc. The smallest SMD crystals are not well-suited for use in VCXOs due to the fact that their C1 values cannot be made large enough for adequate frequency tuning. By using larger crystals, a design can be accomplished that provides for a larger electrode for VCXOs and a smaller electrode for non-tuning oscillators. With the smallest SMD crystals, the best that can be accomplished is optimization for a low R_R value.

There is a relatively constant ratio between C0 and C1, depending upon how efficiently the electrodes are driving the piezo properties of the quartz. The lower the C0/C1 ratio, the more efficiently the piezo properties are used. Large metal crystals usually have the best efficiency with a C0/C1 ratio close to 200. Small ceramic surface mount crystals perform more poorly with a C0/C1 ratio around 400.

Overtones

A singular quartz crystal can vibrate at a variety of different harmonics. The most common vibration is the “fundamental mode”. This mode is the 1st harmonic and the lowest resonance frequency. Overtones appear at odd multiples of the fundamental mode frequency. For example, there is a 3rd overtone, a 5th overtone, etc. Each overtone can be represented with an extra C1-L1- R_R branch in the crystal model. Generally, the higher the overtone, the higher the R_R will be for that overtone. This is most accurate at the lowest (3rd and 5th) overtones. Typically, a crystal oscillator has more oscillator gain (bigger negative resistance) at lower frequencies and with the R_R values at overtones being bigger, without any additional filtering the crystal oscillator will always oscillate at the fundamental mode frequency. The simplest method to make the oscillator oscillate at the 3rd overtone is a high-pass filter to suppress the oscillator gain near the fundamental frequency. If there is sufficient oscillator gain at the 3rd overtone frequency to overcome the R_R at the 3rd overtone, the oscillator will oscillate at the 3rd overtone frequency. To oscillate at 5th or higher overtones it is recommended to work with a band-pass filter to suppress both higher and lower tones.

The crystal resonance frequency is a function of the quartz plate thickness. To increase the frequency, the quartz plate thickness needs to be reduced. Thinner crystals can be more difficult to handle during the manufacturing process. Using the crystal at an overtone is a compromise that makes the crystal itself less expensive while making the oscillator circuit more complex.

The vibrating mass is the same at an overtone, making the L1 values of the overtones and the fundamental mode approximately the same. That makes the C1 values much smaller, making the frequency higher (theoretically, 9X smaller for the 3rd overtone, 25X smaller for the 5th overtone, etc.). This sort of overtone operation is not suited for VCXO designs.

Inverted Mesa Technology

The inverted mesa technology makes the crystal very thin in the middle portion of the crystal plate. The thicker outer edges allow for easy handling and the thinner center emits a high fundamental mode frequency when the electrodes are placed only inside the thin area.

The inverted mesa technology is relatively expensive, but for some applications it is worth it (VCXO designs at high frequencies, for example). Micrel provides high-frequency VCXO ICs, such as the PL520 and PL586 series, which function with inverted mesa crystals. Additionally, Micrel’s PL686-05 and PL610-01 can also work with the high-frequency inverted mesa crystals.

Drive Level

The power dissipated in the crystal is the drive level. Above a certain drive level, crystals can show nonlinear properties that can cause unwanted side effects. Coupling with an unwanted vibration mode can occur, resulting in certain frequency instabilities. Micrel can specify the drive level coming from the crystal oscillator in the timing IC so that a properly functioning crystal can be selected.

Q-Factor

Compared to discretely built tank circuits with LS and CS, the quartz crystal has a very large Q-factor. This parameter is usually not specified, but often expected, of the quartz crystal. The high Q-factor makes the frequency very stable, but another consequence of the high Q-factor is very low noise in the oscillator signal. The Q-factor of a quartz crystal can easily be above 10,000 and sometimes even above 100,000.

Crystal Frequency Accuracy and Stability

The resonance frequency of a quartz crystal is very stable compared to alternative techniques such as an LC tank or other materials like ceramic resonators. When used properly, a quartz crystal is a very accurate frequency reference for its cost and this is mostly why quartz crystals are so popular. The frequency accuracy and stability can be broken down into several items:

- **Calibration Tolerance at Room Temperature:** This is the accuracy of the frequency at nominal conditions. For purposes of identification, “easy” is $\pm 50\text{ppm}$, “medium” is $\pm 25\text{ppm}$, and “difficult” is $\pm 10\text{ppm}$.
- **Temperature Drift:** Referenced to the frequency at nominal conditions, the frequency drifts with a particular temperature curve. The temperature curve can be modeled with a 3rd order equation and the crystal is usually designed to minimize the drift for a particular temperature range. It is advised to select a crystal that is specified for the same temperature range as what the crystal oscillator circuit will be exposed to. The two most common temperature ranges are industrial (-40°C to $+85^{\circ}\text{C}$) and the commercial (0°C to $+70^{\circ}\text{C}$). The wider industrial temperature range results in bigger drift numbers or can be more difficult to achieve certain drift requirements with. A $<\pm 20\text{ppm}$ drift for the industrial range is considered “difficult”, but it is relatively easy to achieve the same numbers using the commercial range. For the commercial range, a $<\pm 10\text{ppm}$ drift is considered “difficult”.
- **Aging:** The frequency of a quartz crystal slowly drifts with time due to aging. Mechanical stresses relax over time or small traces of oxygen or moisture can react with the electrode and make the crystal heavier. Usually the direction of the frequency drift with aging is down. The crystal will age quickly in the first few years of use, slowing over time. Occasionally, a manufacturer will pre-age crystals at the factory to meet a very tight aging specification. A typical aging specification is 5ppm per year. Sometimes a specification will read as 5ppm for the first year and lower subsequently.
- **Total Stability:** This number includes all of the above and this is actually the most popular method for specifying the frequency accuracy of a quartz crystal. It guarantees that the crystal oscillator frequency does not drift outside a certain range under all conditions and for the life of the device. Total frequency numbers like $\pm 100\text{ppm}$ are relatively easy, even with -40°C to $+85^{\circ}\text{C}$ temperature range. Medium is $\pm 50\text{ppm}$ and below that it quickly gets very difficult. Dealing with a total stability requirement, the crystal manufacturer can optimize the frequency accuracy for each individual item for the best manufacturability.

The Micrel IC itself does not contribute significantly to the accuracy and stability of its output clocks. The accuracy comes from the quartz crystal reference.

Crystal Oscillator Mathematics

This formula provides the relation between the ESR value and R_R value:

$$ESR = R_R \times (1 + C_0/CL)^2$$

Where:

- $R_R = 15\Omega$
- $C_0 = 3\text{pF}$
- $CL = 12\text{pF} \rightarrow ESR = 15 \times (1 + 3/12)^2 = 23\Omega$

The following formula helps calculate frequency movements:

$$FL = FS \times \text{SQRT}(1 + C_1 / (C_0 + CL))$$

The above formula can be used to find the frequency change as a result of a load capacitance change. If CL_1 causes FL_1 and CL_2 causes FL_2 :

$$FL_1/FL_2 = \text{SQRT}((1 + C_1/(C_0 + CL_1)) / (1 + C_1/(C_0 + CL_2)))$$

Simplified: $FL_1/FL_2 = 1 + 2 \times C_1 \times (CL_2 - CL_1) / (C_0 + CL_1) / (C_0 + CL_2)$. When CL_1 and CL_2 are close together:

$$dFL = 2000 \times C_1 \times dCL / (C_0 + CL)^2$$

dFL is the frequency shift, in ppm (parts per million) caused by the load capacitance shift dCL . C_1 is the motional capacitance in fF (femto farad), dCL is the load capacitance shift in pF (pico farad), C_0 is the parallel capacitance in pF, and CL is the nominal load capacitance in pF.

CL Error Example

A crystal is calibrated for $CL = 12\text{pF}$ and the IC spec also says $CL = 12\text{pF}$ but there is an additional 1pF parasitic capacitance in the PCB. How large is the frequency error because of the extra 1pF ? Additional information for the crystal: $C_1 = 8\text{fF}$ and $C_0 = 2.5\text{pF}$. The frequency error $dFL = 2000 \times 8 \times 1 / (2.5 + 12)^2 = 76\text{ppm}$.

VCXO Example

The VCXO specification states:

$$CL1 = 20pF \text{ at } V_{CONTROL} = 0V, CL2 = 8pF \text{ at } V_{CONTROL} = 1.65V \text{ and } CL3 = 4pF \text{ at } V_{CONTROL} = 3.3V.$$

The crystal is calibrated for CL = 8pF so the nominal frequency is achieved at $V_{CONTROL} = 1.65V$. The crystal's parameters are:

$$C1 = 8fF (= 0.008pF) \text{ and } C0 = 2.5pF$$

With the control voltage tuning between 0V and 3.3V, the frequency tuning range can be calculated by:

$$FL1/FL2 = \text{SQRT} \left(\frac{(1+0.008/(2.5+20))}{(1+0.008/(2.5+8))} \right) = 0.999797 = 1 - 203 \text{ ppm}$$

$$FL3/FL2 = \text{SQRT} \left(\frac{(1+0.008/(2.5+4))}{(1+0.008/(2.5+8))} \right) = 1.000234 = 1 + 234 \text{ ppm}$$

The frequency tuning range is $-203/+234ppm$ with 0ppm in the center at $V_{CONTROL} = 1.65V$.

Fine Tuning the Load Capacitance

When the load capacitance of the timing IC is different from the load capacitance the crystal was calibrated to, the crystal oscillator will not oscillate at the intended nominal frequency of the crystal. We can fix that by adding capacitors to the crystal oscillator circuit. For example, adding a capacitor in series with the crystal lowers the load capacitance of the oscillator circuit (Figure 4).

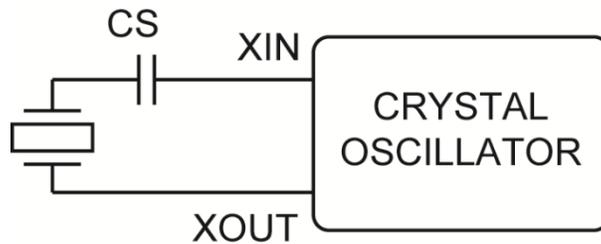


Figure 4. Crystal CL Value is Smaller than Oscillator CL Value

In the event the crystal oscillator load capacitance (CLO) is larger than the load capacitance the crystal is calibrated to (CLX), CS can be added in series to lower the crystal oscillator load capacitance to match the crystal:

$$CS = CLO \times CLX / (CLO - CLX)$$

Where:

- CLO = 14.32pF
- CLX = 12pF → CS = 14.32×12 / (14.32 – 12) = 74pF

When the error is only 2pF or 3pF, a capacitor can be added from XIN to ground to increase the oscillator load capacitance. The problem with this method is that the oscillator gain reduces when adding a capacitor to ground. A more balanced approach is to add a capacitor to ground at both XIN and XOUT (Figure 5).

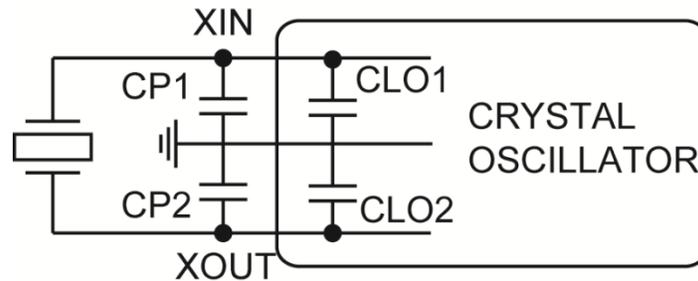


Figure 5. Crystal CL Value is Larger than Oscillator CL Value

Contact Micrel to find out how much capacitance can be added safely in this fashion to a specific Micrel timing IC. The math is not so precise for this case due to there being various ratios for CLO1/CLO2. However in most cases we can assume the values for CLO1 and CLO2 are quite close to one another. To correct the load capacitance 1pF up with CP1 only, CP1 = 4pF (approximately) must be added. To correct the load capacitance 1pF up with CP1 and CP2, CP1 = CP2 = 2pF (approximately) must be added. Using both CP1 and CP2 is the better method that affects the oscillator gain less.

Using a Reference Clock Signal Instead of a Crystal

Most crystal oscillators allow the XIN pin to be driven with a reference clock signal instead of using a crystal. Although this method is acceptable, there are a few items to consider before implementing it:

- The usual signal at XIN is a sine wave with a peak-to-peak signal swing smaller than VDD. When applying a square wave to XIN, higher frequency harmonics will couple through CLO1 (Figure 6) to the ground rail and can interfere with other parts of the circuit. When issues such as deterministic jitter or spurs in the phase noise arise, try and slow down the edges on the reference clock square wave with another series resistor. A value of 100Ω is a good first try.
- Most crystal oscillators have DC biasing inside the IC. When using a large signal reference clock with rail-to-rail signal swing, the XIN pin can be directly driven. Conversely, when the reference clock has a smaller signal swing – a TCXO clipped sine wave, for example – it is advised to use a series coupling capacitor to allow the DC biasing to settle at the intended level.

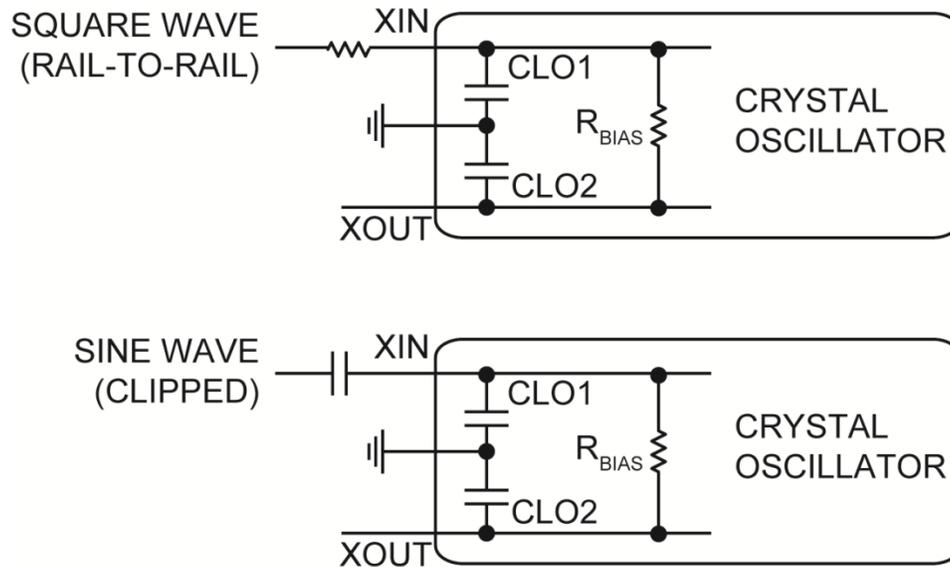


Figure 6. Driving XIN with External Reference Clock

Crystal Selection Checklist

When selecting a crystal for a Micrel timing IC, the following checklist can be used:

- Select the correct nominal frequency.
- Select the desired package type.
- Select the correct load capacitance. Attempt to find a crystal with a load capacitance as close as possible to the load capacitance of the oscillator. Potential frequency error can be calculated from the difference between the crystal oscillator load capacitance and the selected crystal load capacitance. When this error is unacceptable, then tuning the load capacitance with capacitors may be needed.
- Select the required frequency accuracy and stability items in combination with the required temperature range and life time of the device.
- Verify that other parameters of the crystal meet the crystal oscillator requirements:
 - Maximum ESR
 - Maximum drive level
 - Maximum C0
 - In case of frequency tuning, there can be a C1, motional capacitance requirement and/or a maximum C0/C1 ratio requirement.

Specific Micrel IC Recommendations

The following is a list of Micrel ICs with specific notes about the crystal used with these ICs:

- **SM802xxx:** The FLEX SM802xxx products use fundamental mode crystals in the range 11MHz to 30MHz. The load capacitance of the oscillator is 10pF. This is a common value and crystals with this load capacitance will be available on the market. Crystals up to $CL = 12\text{pF}$ can be tuned in by adding capacitors from XIN and XOUT to ground.
- **SM803xxx:** The FLEX2 SM803xxx products use fundamental mode crystals in the range 12MHz to 50MHz. The load capacitance of the oscillator is 12pF. This is a common value. With this oscillator it is not recommended to increase the CL value with capacitors to ground but decreasing the CL value to 10pF or 8pF with a capacitor in series with the crystal is OK.
- **PL135-XX:** The PL135 products are fanout XOs. There will be multiple clock outputs with the crystal frequency. The CL value for the PL135-27 is 12pF, for the -37 is 8pF and for the -47 and -67 is 15pF. The crystal frequency range is 10MHz to 40MHz.
- **PL500-17:** The PL500-17 is a VCXO. The nominal load capacitance at the nominal control voltage is 8pF, at the lowest control voltage is 15pF and at the highest control voltage is 5.2pF. For the frequency to be at the nominal value with the nominal control voltage the crystal CL value needs to be 8pF. The value of the motional capacitance C1 of the crystal determines the frequency tuning range. Formulas from page 6 can be used to calculate the frequency tuning range. The PL500-17 can work with crystals between 17MHz and 36MHz.
- **PL500-37:** The PL500-37 is a VCXO similar to the PL500-17 but designed for higher-frequency crystals in the range 36MHz to 130MHz. Above about 60MHz the crystals are too thin to handle with the common design and it becomes more practical to use inverted mesa technology. The load capacitance at the nominal control voltage is 5.1pF, at the lowest control voltage is 9.5pF and at the highest control is 3.3pF.
- **PL502-3X:** The PL502-3X products are VCXOs with additional PLL to multiply the crystal frequency with up to X32. There is also an output divider that can divide down the crystal frequency, down to divide by 16. The load capacitance at the nominal control voltage is 9.5pF, at the lowest control voltage is 21pF and at the highest control voltage is 6.0pF. The PL502-3X can work with crystals between 12MHz and 25MHz.
- **PL520-XX:** The PL520 products are VCXOs that work with high-frequency crystals. The PL520-20 uses 100MHz to 200MHz crystals, the PL520-30 uses 65MHz to 130MHz crystals and the PL520-80 uses 19MHz to 65MHz crystals.
- **PL586-XX:** The PL586 products are high frequency VCXOs that were designed for super low phase noise. The different ICs work with crystal frequencies between 75MHz and 170MHz with inverted mesa technology. The nominal load capacitance is close to 5pF. These ICs are sold unpackaged and integrated with a quartz crystal into the same hermetically sealed package and the crystal frequency is calibrated when already connected to the IC. This makes it less important to know the exact load capacitance.
- **PL602-2X, PL60203X:** PCIe clock generator ICs that use a 25MHz crystal with a load capacitance of 12pF.
- **PL602-37:** Similar to the PL502-37 (see PL502-3X) but without the VCXO. The crystal oscillator load capacitance is 20pF. This is relatively large but smaller CL values can be achieved by adding a capacitor in series with the crystal.
- **PL602041, PL60208X:** PCIe clock generator ICs that use a 25MHz crystal with a load capacitance of 10pF.
- **PL6070XX:** PCIe clock generator ICs that use a 25MHz crystal with a load capacitance of 15pF.
- **PL610-01:** This clock generator is customizable (factory programmable) and one of the programmable items is the load capacitance for the crystal. The value can be chosen between 8pF and 12pF. The crystal frequency can be between 5MHz and 60MHz.
- **PL610-32:** This is a special low-power clock generator for making an RTC 32.768MHz clock using a 16.777MHz crystal. The load capacitance is only 3pF to keep the power consumption low. Please contact the factory about using larger values.

Specific Micrel IC Recommendations (Continued)

- **PL611-XX**: Customizable clock generators with PLL. The load capacitance of the crystal oscillator can be programmed between 5pF and 20pF. The crystal frequency can be between 10MHz and 30MHz.
- **PL611s-XX**: Customizable clock generators with PLL, similar to PL611-XX but smaller and lower power. The load capacitance of the crystal oscillator can be programmed between 8pF and 12pF and the crystal frequency can be between 10MHz and 50MHz.
- **PL613-XX**: Customizable clock generators with multiple PLLs and multiple outputs. The load capacitance is fixed to 15pF (not programmable). The crystal frequency can be between 10MHz and 50MHz.
- **PL671-XX**: EMI reduction clock generators that can use a crystal between 10MHz and 40MHz. The load capacitance of the crystal oscillator is 15pF.
- **PL686-XX**: Super low-phase noise clock generators that use inverted mesa crystals in the range 75MHz to 170MHz. These ICs are sold unpackaged for integration together with the crystal in a low phase noise clock module.
- **SY89529**: Clock generator that uses a 16.66MHz crystal and the crystal oscillator is a series mode type that runs the crystal near the series resonance. A certain load capacitance value can be achieved with a capacitor in series with the crystal.
- **SY8953X**: Clock generators that use crystals between 14MHz and 18MHz. The crystal oscillator is a series mode type that runs the crystal near the series resonance frequency. Add a capacitor in series to achieve a certain load capacitance value.
- **SM8400XX**: Clock generators that use a 25MHz crystal. This crystal oscillator needs external capacitors from XIN to ground and XOUT to ground to operate properly. The capacitance in the IC is only 2pF and 2 × 20pF external makes CL=12pF or 2 × 30pF external makes CL=18pF. Do not increase above CL = 18pF.
- **SM843256, SM844256**: Clock generators that use crystals between 18MHz and 25MHz with a load capacitance of 12pF.
- **SY898535**: LVPECL fanout buffer that can also use a crystal for the frequency reference input. The crystal frequency can be between 12MHz and 40MHz.

MICREL, INC. 2180 FORTUNE DRIVE SAN JOSE, CA 95131 USA

TEL +1 (408) 944-0800 FAX +1 (408) 474-1000 WEB <http://www.micrel.com>

Micrel makes no representations or warranties with respect to the accuracy or completeness of the information furnished in this data sheet.

This information is not intended as a warranty and Micrel does not assume responsibility for its use. Micrel reserves the right to change circuitry, specifications and descriptions at any time without notice. No license, whether express, implied, arising by estoppel or otherwise, to any intellectual property rights is granted by this document. Except as provided in Micrel's terms and conditions of sale for such products, Micrel assumes no liability whatsoever, and Micrel disclaims any express or implied warranty relating to the sale and/or use of Micrel products including liability or warranties relating to fitness for a particular purpose, merchantability, or infringement of any patent, copyright or other intellectual property right.

Micrel Products are not designed or authorized for use as components in life support appliances, devices or systems where malfunction of a product can reasonably be expected to result in personal injury. Life support devices or systems are devices or systems that (a) are intended for surgical implant into the body or (b) support or sustain life, and whose failure to perform can be reasonably expected to result in a significant injury to the user. A Purchaser's use or sale of Micrel Products for use in life support appliances, devices or systems is a Purchaser's own risk and Purchaser agrees to fully indemnify Micrel for any damages resulting from such use or sale.

© 2014 Micrel, Incorporated.

Revision History

| Date | Change Description/Edits by: | Rev. |
|---------|--|------|
| 7/11/14 | Initial release of ANTC207 application note. – S. Thompson | 1.0 |
| | | |